

Vector Electronics

QuBi

November 17, 2025

The purpose of this article is to describe an attempt to solve electronic circuits made of non-linear devices like diodes, bipolar transistors, JFETs, MOSFETs, etc.

A common approach is to set the circuit at some operating point and wiggle it around with the input signal. For small variations, even the most non-linear device can be approximated by a linear model. The *Small Signal Analysis*, as it is called, is a classical framework for that.

However, some circuits are trickier and make one or more nonlinear devices operate way beyond the small signal hypothesis.

The class AB (push/pull) amplifier is one example: a transistor in the pair goes from cutoff to linear region as the input rises. The other transistor does the opposite. Meanwhile, the output follows the input nicely (the circuit as a whole surprisingly acts as if everything were linear.)

To fully analyse this, one could try to use a full model of the transistor (exponential curve) however:

- the equations usually have no closed-form expression (equations combining $\exp()$ and polynomials)
- it doesn't give much insight on *how* the thing works.

The Piecewise Linear Model

A nonlinear continuous function can always be approximated by a piecewise affine (linear) function¹, provided the model is refined and enough control points are introduced. Thus, when analyzing a circuit, one can quite reasonably assume, as a first approximation, that the characteristic of a nonlinear component is in fact piecewise linear.

The parameters of the linear relationship (slope and offset) may not yet be known for the present operating point, but they must necessarily correspond to one of the (slope, offset) pairs among those defined in the proposed piecewise affine model.

¹In other words, the set of piecewise linear functions is dense in the space of continuous real-valued functions

The task then reduces to determining which pair applies at a given operating point. The existence of such a pair is "reassured" by the fact that every circuit necessarily has *at least* one operating point. It is reasonable to assume that this solution is unique.²

For most practical cases, the overall result is that every component can be treated as linear, thereby enabling the full use of linear analysis techniques (superposition principle, etc.) without any loss of generality.


Notice that, since any linear transformation to a piecewise linear function is still a piecewise linear function, the very concrete consequence is that the piecewise-affine property of a nonlinear component **propagates** to all the properties of the electronic circuit in which it is embedded.

In this sense, we speak in this paper of a *Vector Analysis* of the circuit. If one views a piecewise-affine function as an element of a vector space (which it is) then the circuit's properties—whatever they may be: V_{OUT} vs V_{IN} , I/V characteristic, transmittance, input impedance, etc.—are likewise contained within that same vector space.

It may therefore be conceivable to interpret the action of a circuit on a nonlinear component as analogous to a matrix acting on a vector. The idea that a circuit might have a kind of "matrix analogue" is perhaps worth exploring further.

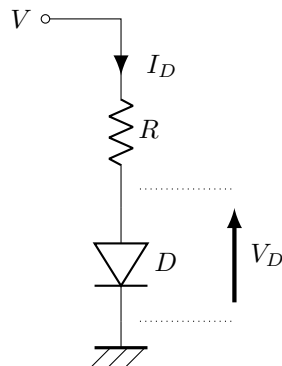Example 1: diode and resistor I

One of the first case study for a diode in a semiconductor lecture is the resistor-diode circuit. It corresponds to most of the LED polarisation circuits.



Even though this is probably the simplest circuit involving a diode, the exponential behaviour of the I/V curve takes a bit of method to solve the circuit.

Here are some common approaches:

- Assume $V_D = 0.7V$ (or a few Volts for LEDs), determine R for a target current (say $5mA$) → Done! It's precise enough for most applications.
- Iterative solving:

²Even though certain "pathological" circuits (e.g. with feedback) may admit multiple possible operating points (stable or not). We will return to this point later.

1. Assume a *guess* voltage $V_D = 0.7V$ across the diode (no need to be accurate)
2. Determine the current I_D using the diode I/V model: $I_D = I_S \left(\exp \left(\frac{V_D}{V_T} \right) - 1 \right)$
3. Calculate the new V_D : $V_D = V - RI_D$
4. Go back to 2. until V_D and I_D eventually settle.


Convergence rate is insanely fast and the result gets accurate to a few digits after only 2 or 3 iteration. However, this method is more of a theoretical fact. It might be useful in a simulator, but for practical situations it won't bring much more precision. The natural dispersion in I/V curves within the same batch of diodes, the lack of detailed information about the model (*e.g.* I_S), not even mentioning the limits of the model itself lowers the benefit of this method.

- Solve using Lambert's W function This function pops naturally when solving equations like $\exp(x) = ax + b$. Though the conclusions are similar to the iterative method.

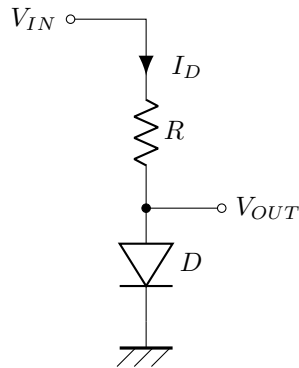Example 2: diode and resistor II

This is a slight variation of the previous diode circuit.

We now have a varying voltage source as input of the system, the diode voltage is the output. We want to see how the output varies with the input (assuming no current is drawn from the output).



For $V_{IN} > 0.7V$ a first good approximation is $V_{OUT} \simeq 0.7V$ regardless of the input voltage V_{IN} .

It makes sense: for an increasing V_{IN} , the diode voltage cannot follow the input and rise as much: the exponential law would kick in and cause a massive increase in current, thereby reducing the diode voltage (through the resistor), opposing the initial voltage increase.


In a way, the diode voltage **does not** want to change. It is the basis principle of Zener diode voltage regulators (although it makes the diode work in a different region—reverse breakdown—but the consequences are exactly the same).

Can we be more precise in the way the output gets regulated? Like before, if we just assume $V_D = 0.7V$, there's not much to say. This is where the Piecewise Linear model can become handy.

*** SECTION IS TODO*** .

Example 3: diode and resistor III


Another variation on a theme of a Diode and Resistor circuit. This time, we have 2 resistors, and we don't neglect the output current anymore.

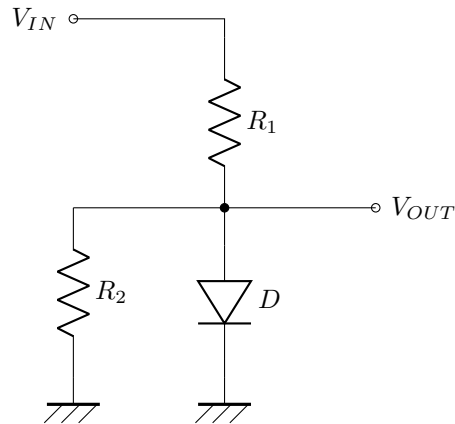

Example 4: the Common Collector (or *Emitter Follower*)


Derivation

For the BJT, we use the following model:

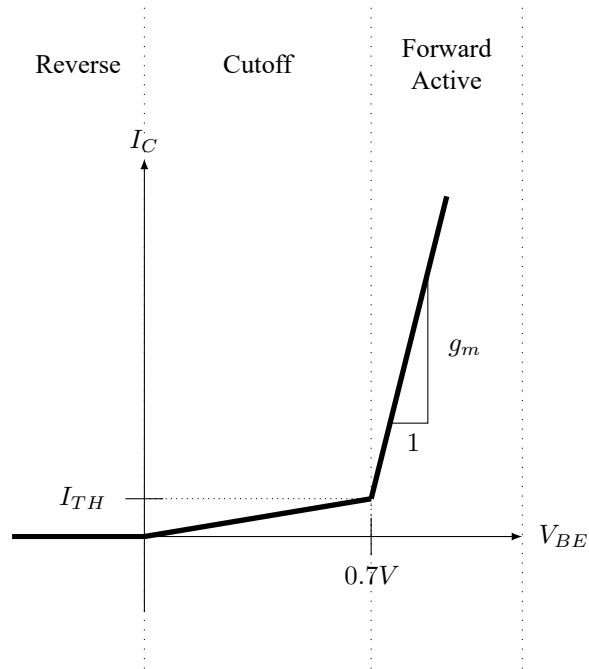

As we will see, for the common collector, the actual values for g_m and I_{TH} do not matter that much. However, this is not true in the general case. We will illustrate that in later examples.

The Common Collector circuit:

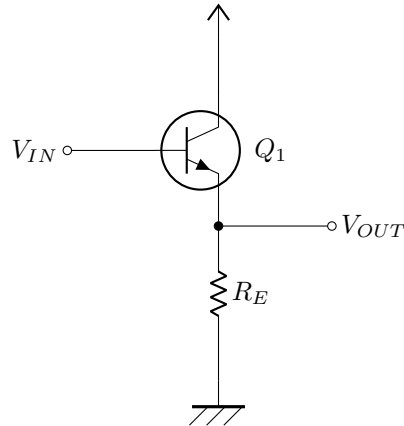

So just like we did with the diode previously: we assume a linear model $I_C = f(V_{BE}) = aV_{BE} + b$ with a and b depending on the operating point (Reverse, Cutoff, Forward Active).

$$V_{OUT} = R_E f(V_{IN} - V_{OUT}) = aR_E (V_{IN} - V_{OUT}) + b$$

Rearranging for V_{OUT} :

$$V_{OUT} = \frac{aR_E}{1 + aR_E} V_{IN} + \frac{b}{1 + aR_E}$$

A BJT is an op amp in disguise.

We've just seen that a BJT in the common emitter arrangement is basically always 'on'. It's the very high transconductance past the $V_{BE} = 0.7V$ that makes all the system work.

Applying a very high gain to a voltage difference reminds us of op amps. Under the hood, an op amp is voltage difference amplifier with a massive gain ($> 10^6$)

The high gain is rarely used as such because it is not very predictable, controlled and uniform in frequency. We much prefer to use this 'unreliable' gain in a feedback loop. It reduces the amplification, but it is more robust to part to part fluctuation


Example 5: the Rubber Diode

Description

In a Class AB Amplifier, we need to 'pre-heat' the NPN and PNP transistors of the final stage. This allows a quiescent current to flow at rest and maintain both transistor in active region. It is mandatory to get rid of the *crossover distortion*.

The polarisation is done usually with 2 diodes in series. But for more flexibility, one can also use the *Rubber Diode* below.

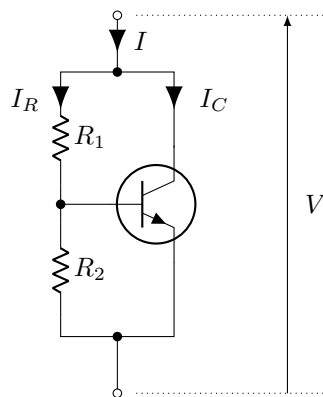It is quite common to have a potentiometer for the resistors R_1 and R_2 to fine-tune the voltage V .



Derivation

Just like with the examples before, we can ignore the base current as a first approximation.

$$\begin{aligned} I &= I_R + I_C \\ &= \frac{V}{R_1 + R_2} + f \left(\frac{R_2}{R_1 + R_2} V \right) \\ &= \frac{V}{R_1 + R_2} + a \frac{R_2}{R_1 + R_2} V + b \\ &= \frac{1 + aR_2}{R_1 + R_2} V + b \end{aligned} \tag{1}$$


The solution is more straightforward as there is no feedback involved here. Observations:

- starts to act as a diode when $\frac{R_2}{R_1 + R_2} \simeq 0.7V$
- when active, the new transconductance becomes $\hat{g}_m = \frac{1 + g_m R_2}{R_1 + R_2}$

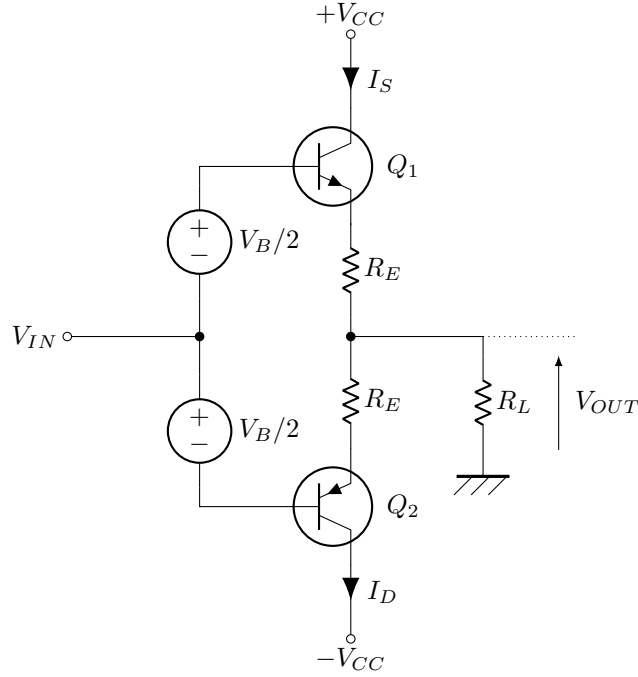Example 6: the Class AB Amplifier

The Class AB Amplifier (or *Push-Pull*) is the typical output stage for many IC devices (op amps, audio amplifiers, etc.) It shows up anytime there is a need to drive a load with some power.

We present here below a simplified view of the circuit in its most general case (with emitter resistors). The polarisation stages are abstracted as simple voltage sources (it doesn't matter much for now).



Derivation

We assume that the base current are negligible.

We denote the collector currents as $I_C = f_S(V_{BE})$ for the NPN and $I_C = f_D(V_{EB})$ for the PNP.

V_B (the bias voltage) is usually around $2V_{BE} \simeq 1.4V$ or above.

V_{IN} is the amplifier's input voltage, we treat it as a static voltage source and we will try to derive the output voltage from it.


We focus on audio applications, so as first approximation the load R_L is essentially ohmic, and usually low impedance (8 to 32 Ω range).

Then, applying the usual KVL and KCL:

$$\begin{cases} I_S = f_S \left(V_{IN} - V_{OUT} + \frac{V_B}{2} - R_E I_S \right) \\ I_D = f_D \left(-(V_{OUT} - V_{IN}) + \frac{V_B}{2} - R_E I_D \right) \\ V_{OUT} = R_L (I_S - I_D) \end{cases}$$

This time, the equations are trickier: the unknowns I_S , I_D and V_{OUT} are all intertwined. I_S depends on I_S (feedback) and V_{OUT} , but V_{OUT} itself depends on I_S ...

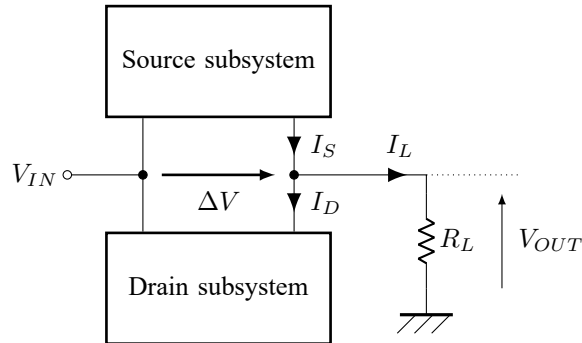
To solve it, we can first try to simplify the whole schematic and see it as being made out of 2 independant subsystems:



Now we can focus on each system and solve them individually.

Class AB subsystem: the current source

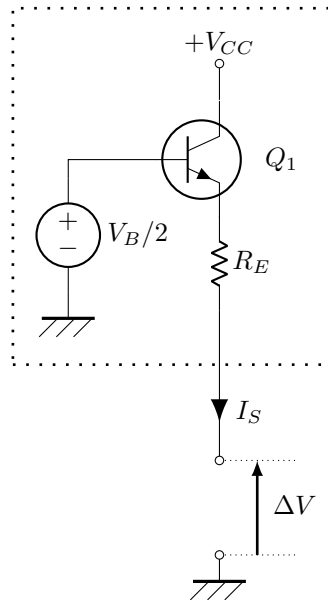Following the way we split the schematic, the Source Subsystem would look like this:



The source current I_S is then expressed as:

$$I_S = f_S \left(-\Delta V + \frac{V_B}{2} - R_E I_S \right)$$

Under a linear model assumption $f_S(V) = aV + b$, we can write that:

$$I_S = a \left(-\Delta V + \frac{V_B}{2} - R_E I_S \right) + b$$

Finally, after a bit of algebra:

$$I_S = -\frac{1}{R_E} \frac{aR_E}{1 + aR_E} \Delta V + \frac{a \frac{V_B}{2} + b}{1 + aR_E} \triangleq \hat{f}_S(\Delta V)$$

We can treat the Source Subsystem as a *virtual* device with its own $I_S = \hat{f}_S(\Delta V)$ transfer curve. And since we assumed a piecewise linear model for the BJT, this device exhibits a piecewise linear characteristic curve too.

To explicit it, let's apply a voltage ΔV in the range $-2.0V \dots 2.0V$, evaluate I_S using the equation above and pick the gain/offset pair $(a(\Delta V), b(\Delta V))$ that works.


BJT Mode	Gain/Offset	$I_S = \hat{f}_S(\Delta V)$
Reverse	$\begin{cases} a = 0 \\ b = 0 \end{cases}$	$I_S(\Delta V) = 0$
Weak Forward	$\begin{cases} a = \frac{I_{TH}}{V_{TH}} \\ b = 0 \end{cases}$	$I_S(\Delta V) = \frac{-a}{1 + aR_E} \left(\Delta V - \frac{V_B}{2} \right)$
Forward	$\begin{cases} a = g_m \\ b = I_{TH} - g_m V_{TH} \end{cases}$	D

Using continuity at $V_{BE} = V_{TH}$, we get:

Note: if you want to try this device experimentally, do not do it by imposing ΔV directly and measuring I_S ; the relationship is too sensitive and that would yield imprecise results. It is better to drain a controlled current instead, and measure the voltage ΔV .

Class AB subsystem: the current drain

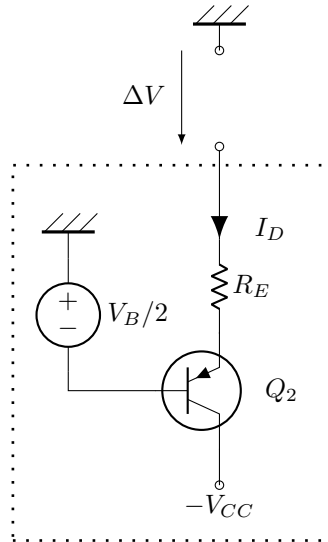Similarly, we extract the lower half of the circuit:



The equation looks like the one we got for the current source version:

$$I_D = f_D \left(\Delta V + \frac{v_B}{2} - R_E I_D \right)$$

And:
$$I_D = \frac{1}{R_E} \frac{a R_E}{1 + a R_E} \Delta V + \frac{a \frac{V_B}{2} + b}{1 + a R_E} = \hat{f}_D(\Delta V)$$

Class AB subsystem: summary


Let's see now how we can combine the subsystems to solve for the class AB entirely. If we treat these subsystems as a *virtual device* (nonlinear) the original system of equation becomes much simpler:

$$V_{OUT} = R_L \left(\hat{f}_S(v_{IN} - v_{OUT}) - \hat{f}_D(v_{OUT} - v_{IN}) \right)$$


Notice that now, I_S and I_D are no longer defined recursively, and also the v_B and R_E terms are integrated in the nonlinear functions $\hat{f}_S$ and $\hat{f}_D$

Example 7: the Differential Pair

The Differential Pair (or Long Tailed Pair □) is the bread and butter of Operational Amplifiers.

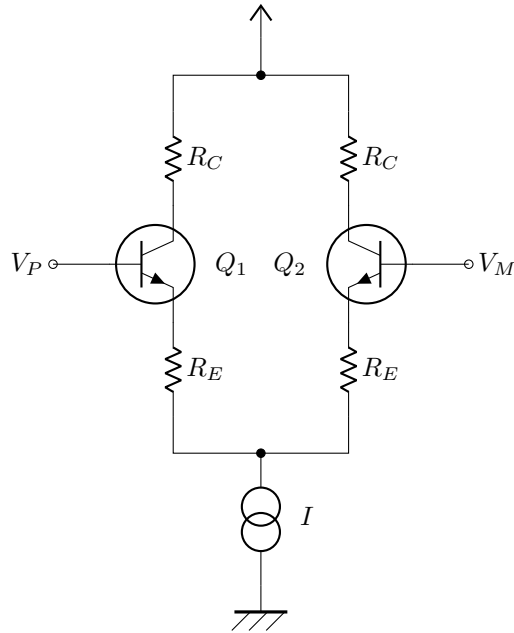

Example 8: the Ring Modulator

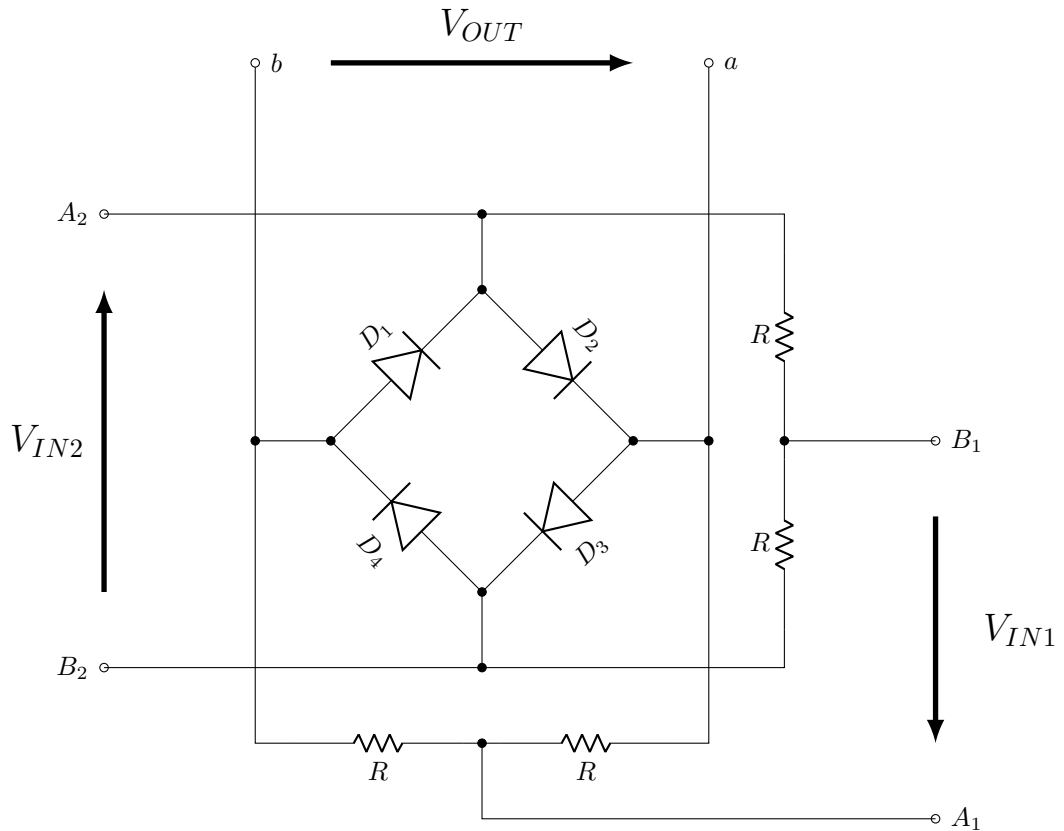

Example 9: the Gilbert Cell (analog multiplier)

That's a tough one, be patient...


Example 10: the Moog Ladder Filter

Description

The Moog Ladder Filter is a parametric low-pass filter used in analog synthesizers.

Its cutoff frequency can be freely adjusted using a control current, which makes it a very unique kind of filter. It gained its popularity and fame in the Moog Synthesizers, as early as the seventies. The term *Ladder Filter* comes from the way the schematic looks: its very much *ladder-like*.

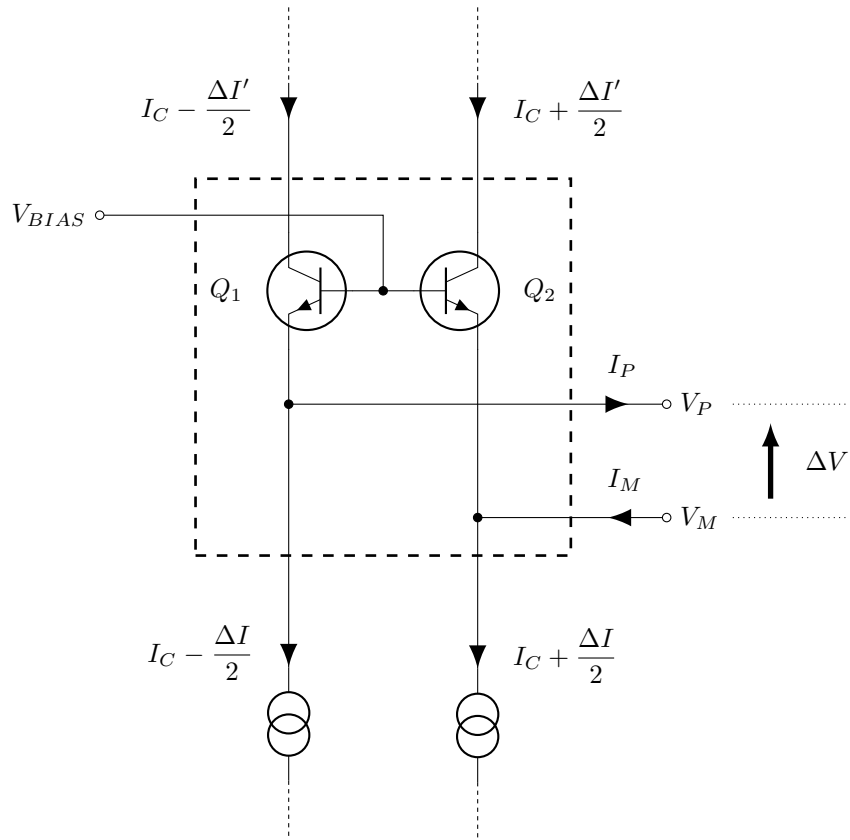The full circuit might look intimidating at first. Let's zoom in on its building block:



This building block can be seen as a **current transformation core**. A balanced current is drawn from the bottom section, and another pair of currents emerges from the top section.

The bottom currents are imposed. We don't know the top currents yet, but considering the symmetry of the circuit, it makes sense to denote them as a differential mode current too: $I_C \pm \frac{\Delta I'}{2}$.

The current drawn from the bottom of the block has specific properties:


- A **control** current I_C applied in common mode
- A **signal** current $\frac{\Delta I}{2}$ applied in differential mode.

Such source is straightforward with the Differential Pair studied earlier.

Let's analyse how the circuit behaves as we load it:

- $I_P = I_M \triangleq I$
- $V_P - V_M \triangleq \Delta V$.

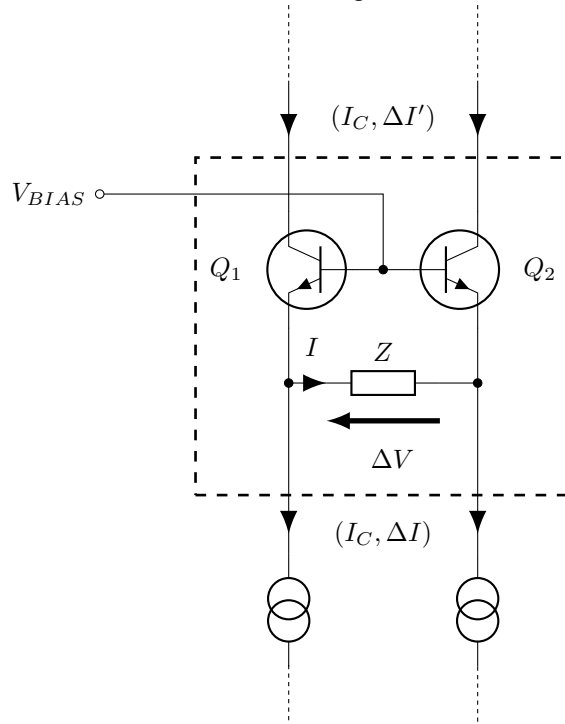If we denote (I, i) as a current pair of common mode current I and differential mode $i/2$, the schematic can be further simplified to:



Now the questions are essentially:

- What is the differential current transfer function $\Delta I' = H(\Delta I)$?
- What is voltage transfer function $\Delta V = G(\Delta I)$?

Output Voltage derivation

As usual we denote the collector current I_C as $I_C = f(V_{BE})$. We neglect the contribution of the base current and assume the transistors have similar properties.

With KCL we get:

$$\begin{cases} I_P = f(V_{BIAS} - V_P) - I_C + \frac{\Delta I}{2} \\ I_M = -f(V_{BIAS} - V_M) + I_C + \frac{\Delta I}{2} \end{cases}$$

With the piecewise linear assumption it becomes:

$$\begin{cases} I_P = -aV_P - I_C + \frac{\Delta I}{2} + aV_{BIAS} + b \\ I_M = aV_M + I_C + \frac{\Delta I}{2} - aV_{BIAS} - b \end{cases}$$

Once loaded, summing the 2 equations gives:

$$2I = -a\Delta V + \Delta I$$

If the load is a simple impedance Z , then $I = \frac{\Delta V}{Z}$. Also, remember that a is the gain in the $I_C = f(V_{BE})$ relationship, therefore it can be seen as an inverse resistance (the *dynamic* resistance).

So we can write $a \triangleq \frac{1}{R_C}$, we get this rather *nice* expression:


$$\Delta V = \left[\frac{(2R_C)Z}{(2R_C) + Z} \right] \frac{\Delta I}{2}$$

Which is also known as:

$$\Delta V = (2R_C // Z) \frac{\Delta I}{2}$$

This is an elementary $V = RI$ relationship!

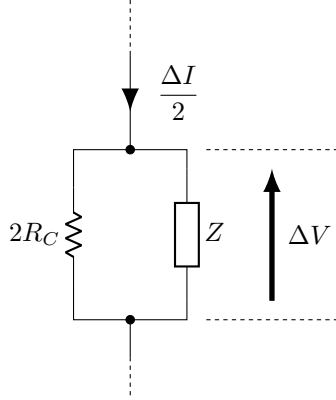So from the load's perspective, it's as if it were stimulated with the signal (differential current ΔI), parallel to some resistance $2R_C$ that depends on the transconductance of $Q1$ and $Q2$ (*i.e.* the gain a in the piecewise linear model).



Comparison without active loading

To fully understand this result, we now study what would happen without the transistors.

Output current derivation

We've established that:

$$\begin{cases} I_P = f(V_{BIAS} - V_P) - I_C + \frac{\Delta I}{2} \\ I_M = -f(V_{BIAS} - V_M) + I_C + \frac{\Delta I}{2} \end{cases}$$

The output current $\Delta I'$ is defined by :

$$\begin{cases} I_C - \frac{\Delta I'}{2} = f(V_{BIAS} - V_P) \\ I_C + \frac{\Delta I'}{2} = f(V_{BIAS} - V_M) \end{cases}$$

Combining the 2 systems of equations we get:

$$\begin{cases} \frac{\Delta I'}{2} = \frac{\Delta I}{2} - I_P \\ \frac{\Delta I'}{2} = \frac{\Delta I}{2} - I_M \end{cases}$$


Summing the 2 finally gives: $\Delta I' = \Delta I - 2I$

With a load impedance Z it follows that:

$$\begin{aligned} \Delta I' &= \Delta I - \frac{2}{Z} \Delta V \\ &= \Delta I - \frac{2}{Z} (2R_C // Z) \frac{\Delta I}{2} \\ &= \left(1 - \frac{2R_C}{2R_C + Z} \right) \Delta I \\ &= \frac{Z}{2R_C + Z} \Delta I \end{aligned} \tag{2}$$

So finally the differential current transfer function: $\Delta I' = \frac{Z}{2R_C + Z} \Delta I$

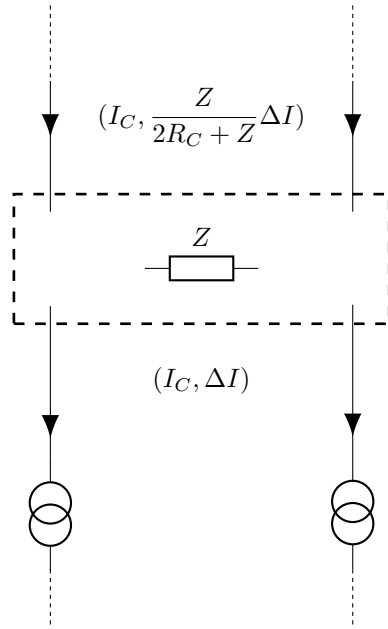We can update the abstract schematic view in terms of *current transformation*:



From which we can derive 2 regimes:

- $R_C \gg |Z|$ (low I_C): $\Delta I \rightarrow 0$
- $R_C \ll |Z|$ (high I_C): $\Delta I \rightarrow \Delta I$ (no change)

Let's get more precise. The dynamic resistance (so the gain in the I/V curve) R_C can be expressed explicitly as a function of I_C therefore giving a more refined description of the transfer curve.

For a BJT:





$$\begin{aligned}
 a &= \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{V_{BE}=V_{BE}^0} \\
 &= \left. \frac{\partial}{\partial V_{BE}} \right|_{V_{BE}=V_{BE}^0} I_S \exp() \\
 &= \left(1 - \frac{2R_C}{2R_C + Z} \right) \Delta I \\
 &= \frac{Z}{2R_C + Z} \Delta I
 \end{aligned} \tag{3}$$

Limits

Large signal analysis

Unlike the Emitter Follower, there's no feedback here to rely on. Hence, we expect deviation from the model if the input is too wide.

Mismatch

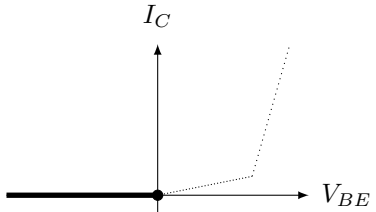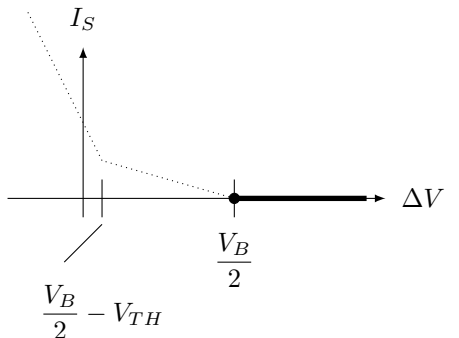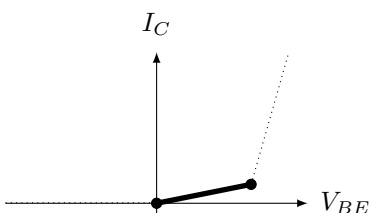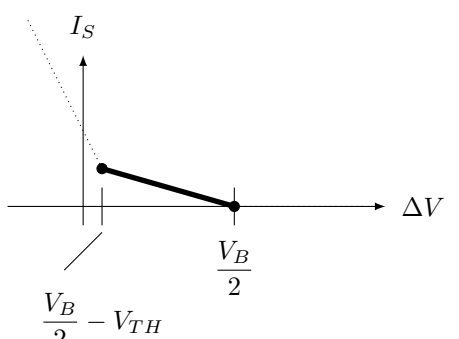BJT Mode	BJT Curve	Source Subsystem
Reverse		
Weak Forward		
Forward	