
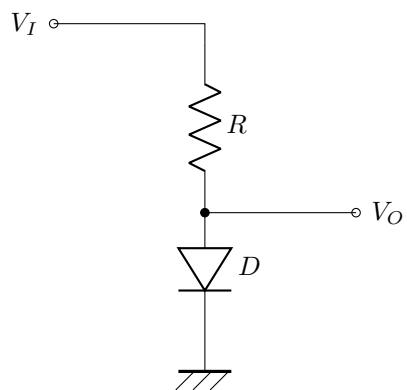


Example 1: diode and resistor I

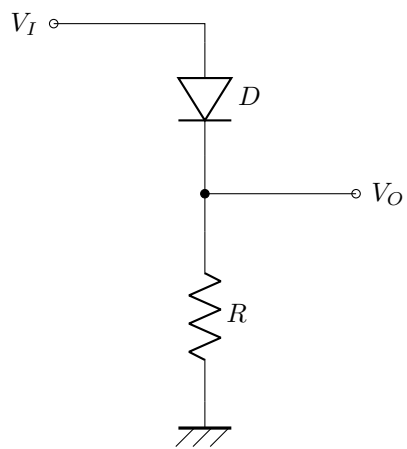

Example 2: diode and resistor II



Example 3: 1 diode and 2 resistors

